

实验一 运算器与存储器

2024春

zjx@ustc.edu.cn

实验目标

- 熟练掌握算术逻辑单元 (ALU)、寄存器堆 (RF) 和存储器的功能、时序及其应用
- 掌握数据通路和控制器的设计和描述方法
- 了解查看电路性能和资源使用情况


实验内容

- 设计算术逻辑单元(Arithmetic and Logic Unit, ALU)和寄存器堆(Register File, RF)
- 比较分布式和块式存储器的特性
- 利用ALU和存储器，设计排序器(Sorter, SRT)

算术逻辑单元

- **src0, src1**: 两操作数, 32位
- **op**: 运算功能, 4位
- **res**: 运算结果, 32位


op	res	功能说明
0	$\text{src0} + \text{src1}$	加
1	$\text{src0} - \text{src1}$	减
2	$\text{src0} <_s \text{src1}$	有符号小于
3	$\text{src0} <_u \text{src1}$	无符号小于
4	$\text{src0} \& \text{src1}$	与
5	$\text{src0} \text{src1}$	或
6	$\sim(\text{src0} \text{src1})$	或非
7	$\text{src0} \wedge \text{src1}$	异或
8	$\text{src0} \ll \text{src1}[4:0]$	左移
9	$\text{src0} \gg \text{src1}[4:0]$	逻辑右移
10	$\text{src0} \ggg \text{src1}[4:0]$	算术右移
11	src1	赋值

 

```
module alu (  
    input [31:0] src0,    //操作数0  
    input [31:0] src1,    //操作数1  
    input [3:0] op,       //运算功能  
    output [31:0] res     //运算结果  
);
```

寄存器堆

```
module rf (  
    input clk,                //时钟  
    input [4:0] ra0, ra1,     //读地址  
    output [31:0] rd0, rd1,   //读数据  
    input [4:0] wa,           //写地址  
    input [31:0] wd,          //写数据  
    input we                  //写使能  
);  
    reg [31:0] x[0:31];       //寄存器堆  
  
    assign rd0 = x[ra0];      //读操作  
    assign rd1 = x[ra1];  
  
    always @(posedge clk)  
        if (we) x[wa] <= wd; //写操作  
endmodule
```

 


- ra0, rd1: 异步读端口0
- ra1, rd1: 异步读端口1
- wa, wd, we: 同步写端口
- clk: 时钟

存储器

```
module mem #(
    parameter DATA_WIDTH = 32,
               ADDR_WIDTH = 10,
               INIT_FILE = ""
)(
    input clk,                                // clock
    input [ADDR_WIDTH-1:0] addr,              // address
    input [DATA_WIDTH-1:0] din,               // data input
    input we,                                 // write enable
    output reg [DATA_WIDTH-1:0] dout         // data output
);
    reg [DATA_WIDTH-1:0] ram [0: (1 << ADDR_WIDTH) - 1];

    initial $readmemh(INIT_FILE, ram); // initialize memory

     always @(posedge clk) begin
        dout <= ram[addr];
        if (we) ram[addr] <= din;
    end
endmodule
```



- Flow Navigator >> Project Manager >> Language Templates
 - Verilog >> Synthesis Constructs >> Coding Examples / Example Modules >> RAM

存储器IP核

- **Vivado**中有存储器IP核可以直接例化使用
- 两种IP类型：分布式(**Distributed**)、块式(**Block**)存储器
- 定制化方式：**ROM/RAM**、单端口/简单双端口/真正双端口等


存储器IP核例化

- **Flow Navigator >> Project Manager >> IP Catalog**
 - Memories & Storage Elements >> RAMs & ROMs >> Distributed Memory Generator
 - 或者 Basic Elements >> Memory Elements >> Distributed Memory Generator
 - Memory config >> Memory Type: Single Port RAM
 - RST & Initialization >> Load COE File

例如，单端口分布式存储器

同步写端口：a (地址)，d (数据)，
we (写使能)，clk

异步读端口：a (地址)，spo (数据)

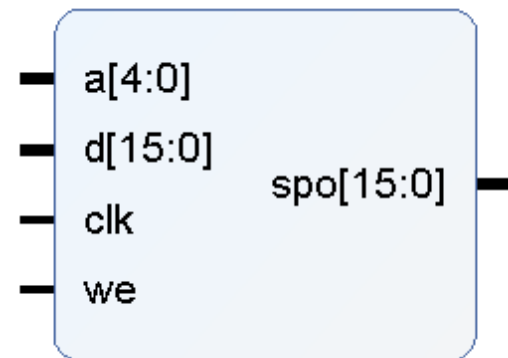

存储器IP核例化 (续)

- **Project Manager – xxxx >> Sources >> IP Sources**
 - IP >> dist_mem_gen_0 >> Instantiation Template >> dist_mem_gen_0.vco

```
dist_mem_gen_0  your_instance_name (  
    .a(a),          // input wire [4:0] a  
    .d(d),          // input wire [15:0] d  
    .clk(clk),       // input wire clk  
    .we(we),         // input wire we  
    .spo(spo)        // output wire [15:0] spo  
);
```

例化模板

COE文件格式

- **An example COE file:**

; Sample Initialization file for a 32x16 distributed ROM

memory_initialization_radix = 16;

memory_initialization_vector =


23f4 0721 11ff ABe1 0001 1 0A 0 逗号或空格分隔每项数据

23f4 0721 11ff ABe1 0001 1 0A 0 (不允许为负数)

23f4 721 11ff ABe1 1 1 A 0

23f4 721 11ff ABe1 1 1 A 0;

分布式存储器IP

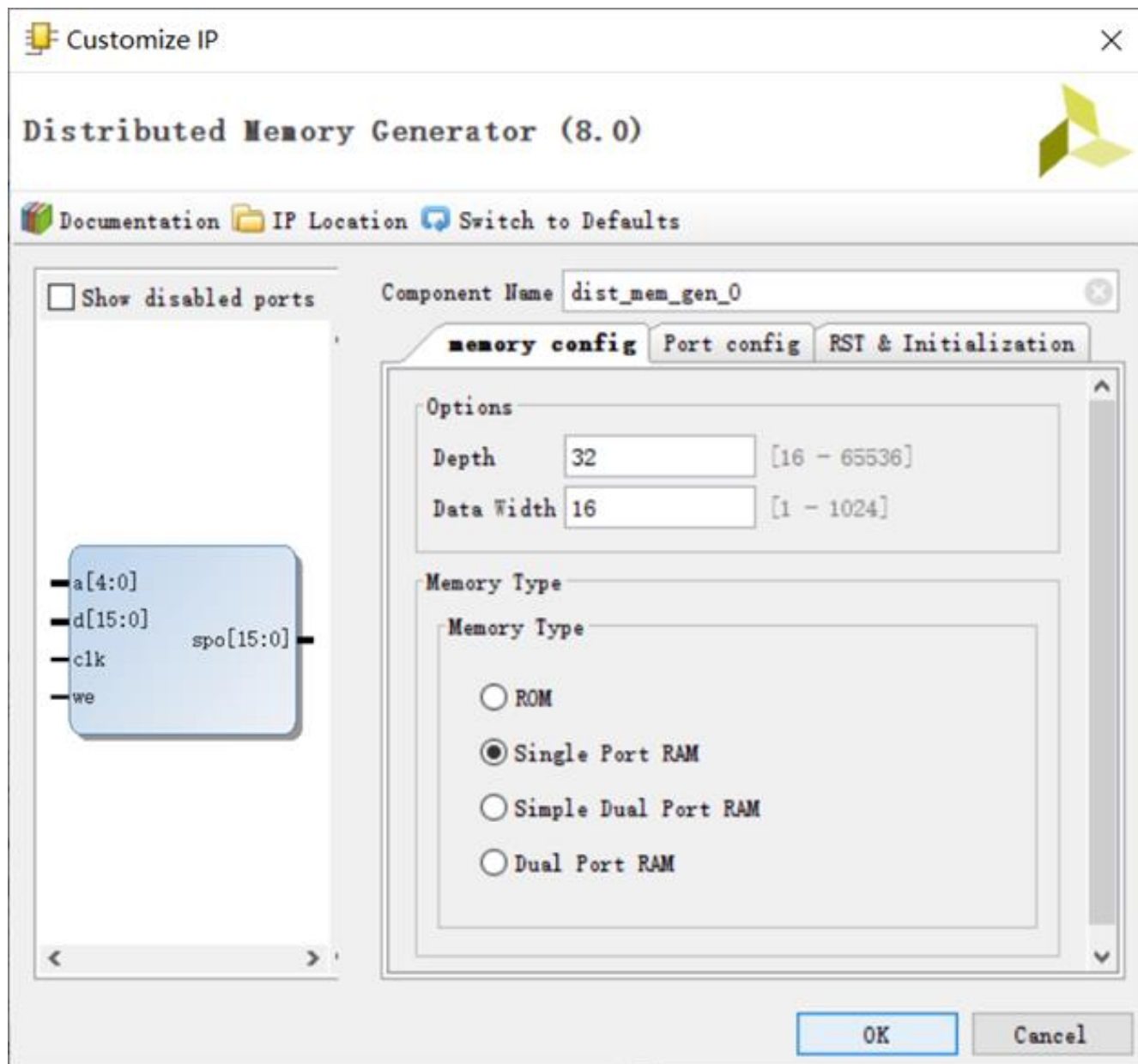

分布式存储器IP

Component Name:

memory config **Port config** RST & Initialization

Input Options

Input Options

☒ Non Registered ☐ Registered

☐ Input Clock Enable ☐ Qualify WE with I_CE

Dual Port Address

Dual Port Address

☒ Non Registered ☐ Registered

Output Options

Output Options

☒ Non Registered ☐ Registered ☐ Both


☐ Common Output CLK ☐ Single Port Output CE

☐ Common Output CE ☐ Dual Port Output CE


Pipelining Options

Pipeline Stages:

分布式存储器IP

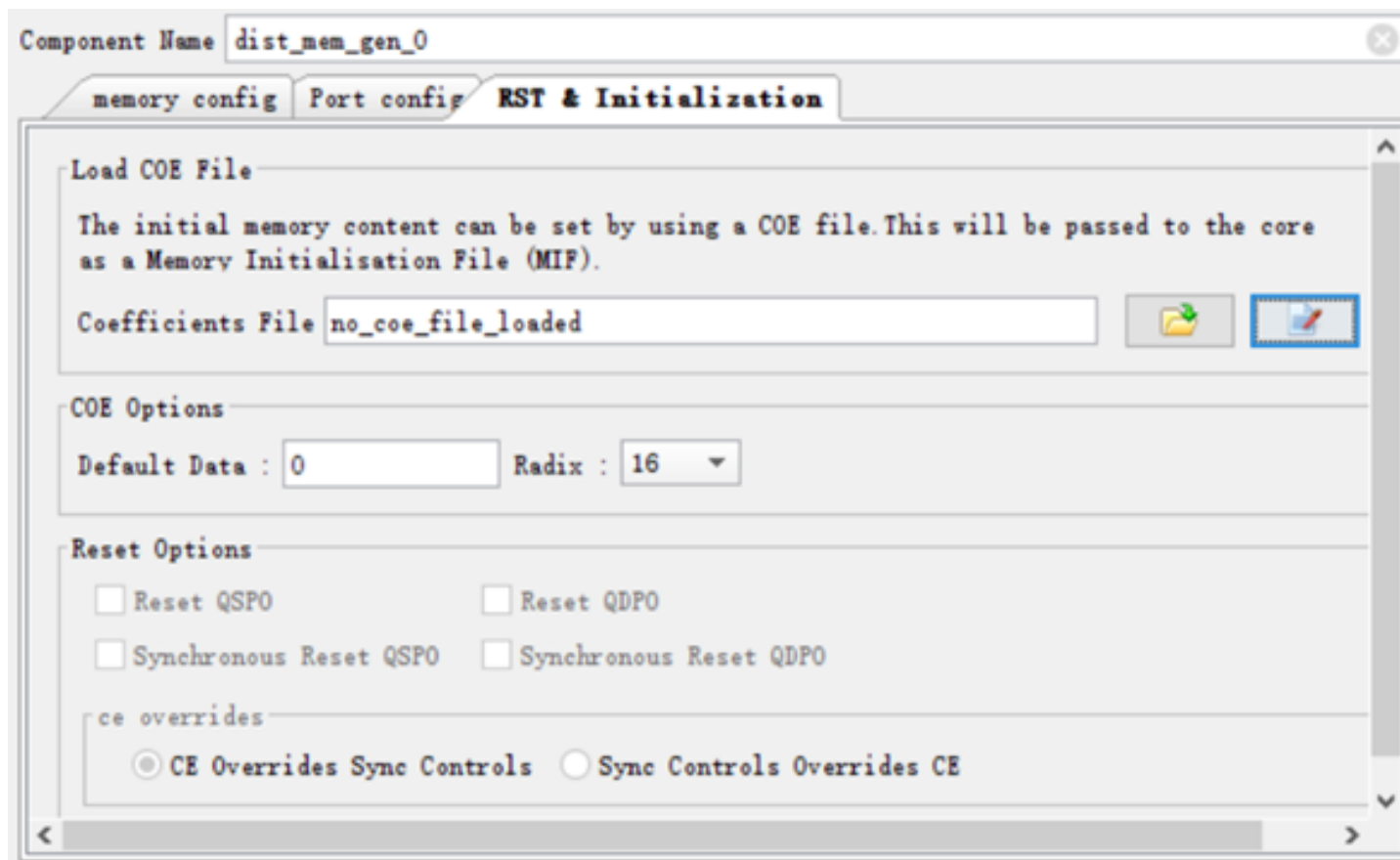

块式存储器IP

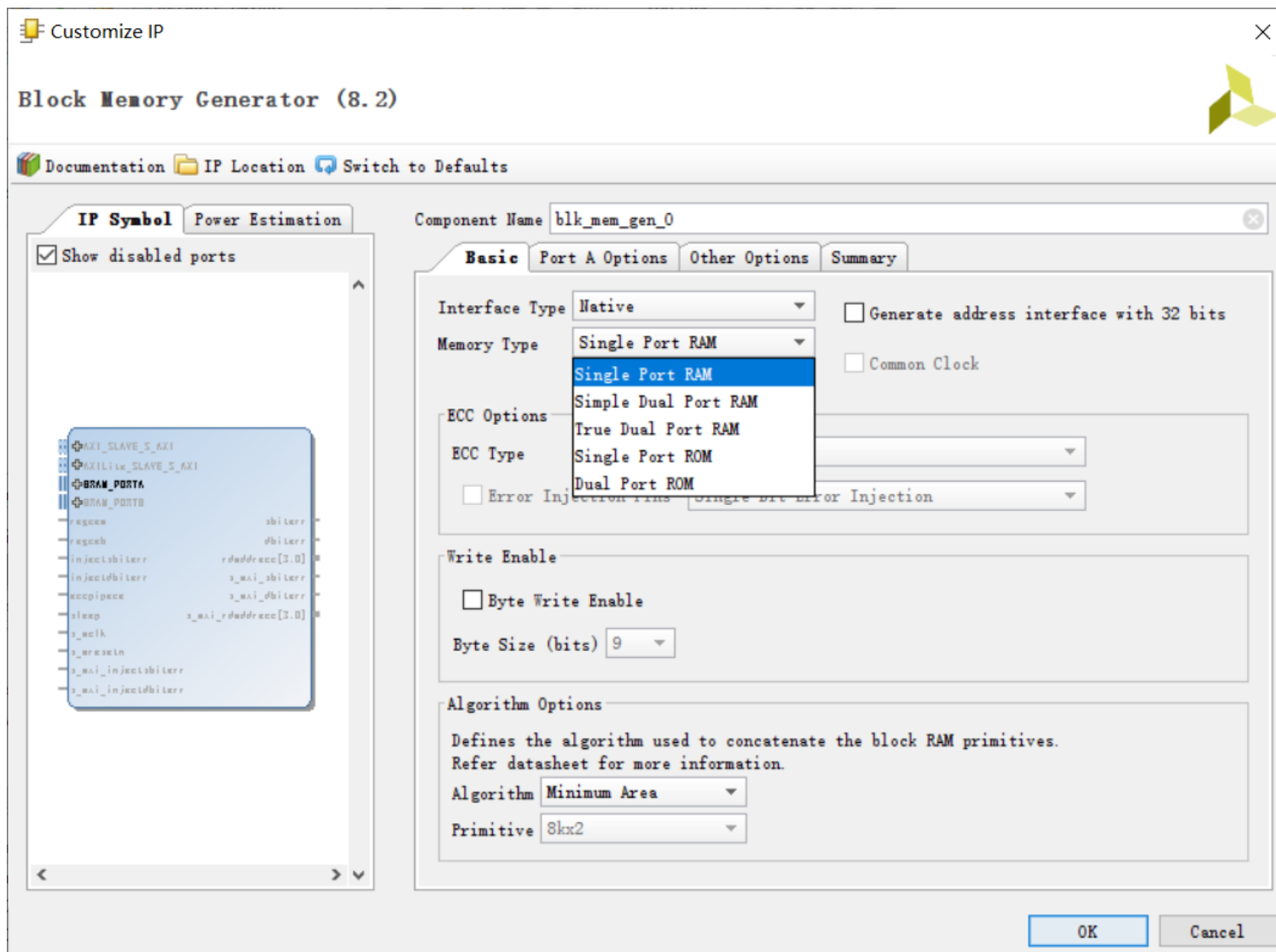

块式存储器IP

Basic **Port A Options** Other Options Summary

Memory Size

Write Width 16 Range: 1 to 4608 (bits)

Read Width 16

Write Depth 32 Range: 2 to 9011200

Read Depth 32

Operating Mode Write First Enable Port Type Use ENA Pin

Port A Optional Output Registers

☐ Primitives Output Register ☐ Core Output Register

☐ SoftECC Input Register ☐ REGCEA Pin

Port A Output Reset Options

☐ RSTA Pin (set/reset pin) Output Reset Value (Hex) 0

☐ Reset Memory Latch Reset Priority CE (Latch or Register Enable)

块式存储器 IP

Basic Port A Options **Other Options** Summary

Pipeline Stages within Mux Mux Size: 2x1

Memory Initialization

☐ Load Init File

Coe File

☐ Fill Remaining Memory Locations

Remaining Memory Locations (Hex)

Structural/UniSim Simulation Model Options

Defines the type of warnings and outputs are generated when a read-write or write-write collision occurs. .


Collision Warnings

Behavioral Simulation Model Options

☐ Disable Collision Warnings ☐ Disable Out of Range Warnings


存储器时序

- Read First Mode

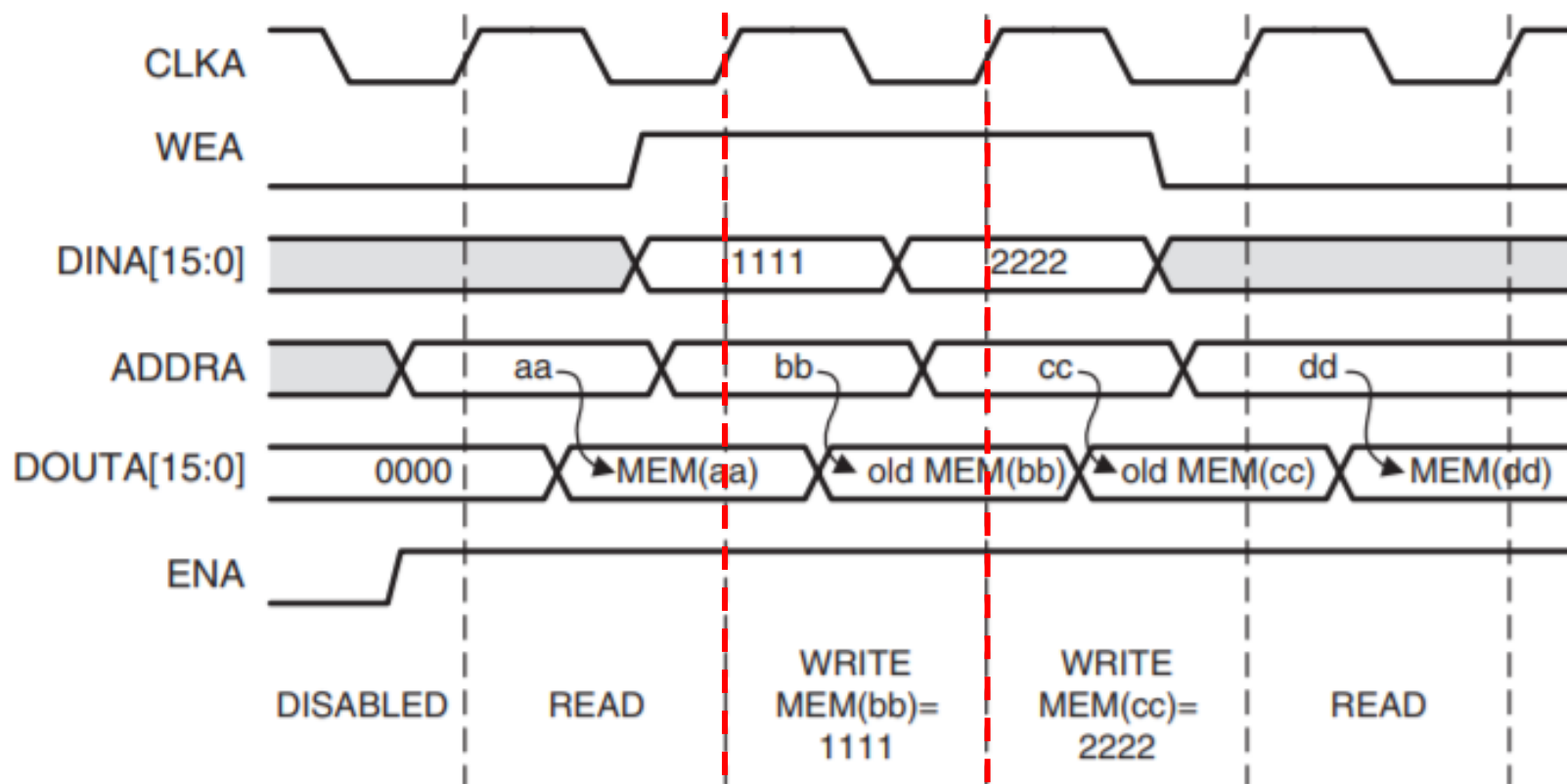


存储器时序 (续)

- Write First Mode

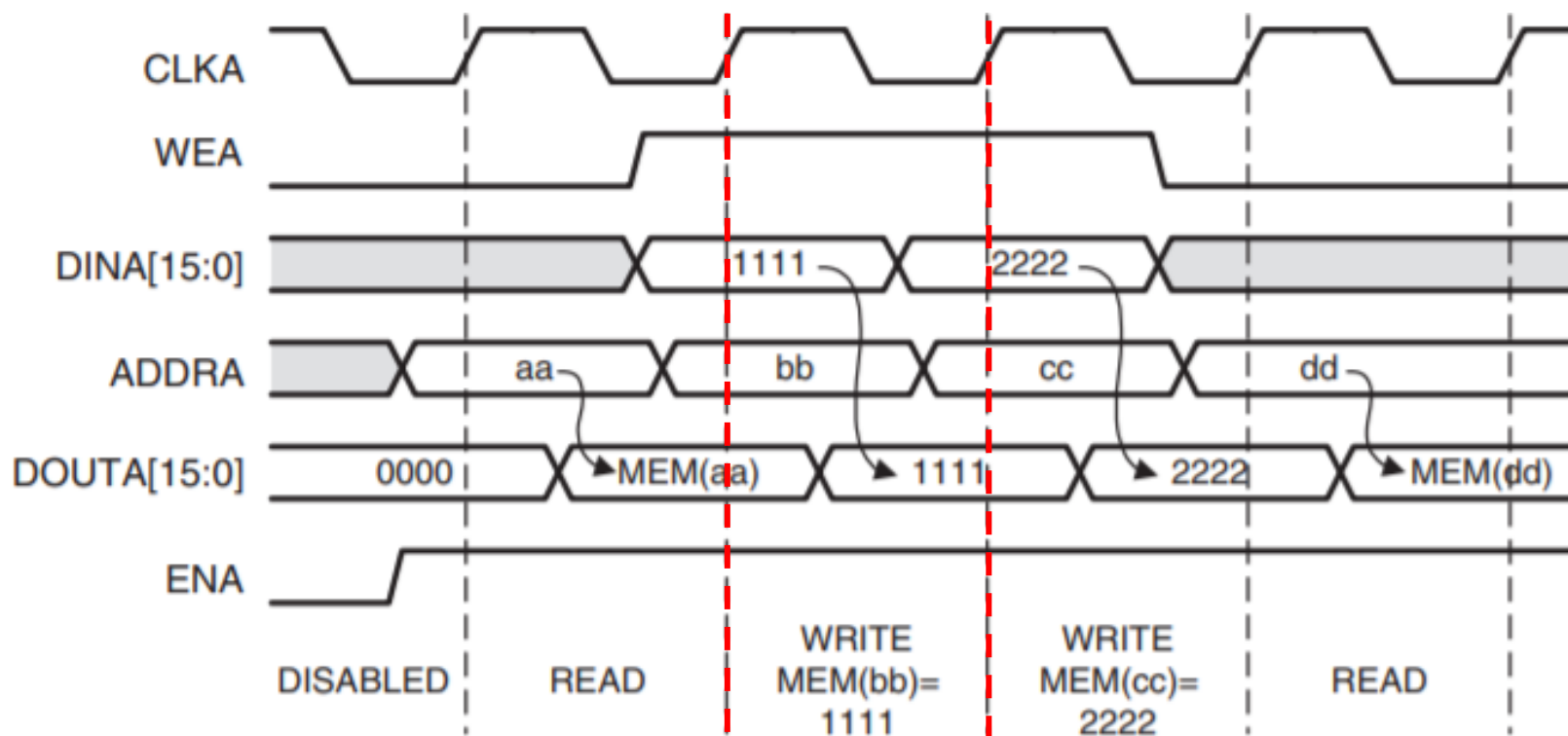

排序器

 - 排序存储器中数据，记录排序所耗时间，查看排序结果
 - up: 0 -- 降序，1 -- 升序
 - start: 启动排序
 - prior: 查看前一个数据
 - next: 查看后一个数据
 - done: 排序结束标志
 - index: 输出数据序号
 - data: 输出数据
 - count: 时钟周期数
 - clk, rstn: 时钟，复位




排序器 (续)

- 工作过程

- 复位后, $done = 1$, $index = count = 0$
- 启动排序后, $done = 0$, $count$ 递增计数;
- 排序结束后, $done = 1$, $count$ 停止计数;
- 通过 $prior$ 或 $next$, 依次查看数据


- 实现要求

 - 存储器类型: 分布式单端口
- 存储器容量: 1024×32 位
- 数据类型: 32 位无符号数
- 排序算法: 冒泡排序
- 用 ALU 实现待排序数据的比较



示例：数列计算器

 
- 利用ALU和RF，设计数列计算器(Series Calculator, SC)
- 工作过程
 - 输入运算符(f)和初始项(q_1, q_2), 存入RF中x0 ~ x2
 - 通过d和en依次分时输入
 - 计算数列后续项, 存入RF中x3 ~ x31
 - $q_n = q_{n-2} \oplus q_{n-1}, n = 3 \sim 31$
 - f 运算功能由ALU定义
 - 输出RF中内容
 - q, n: 输出数据和序号
 - pri, nxt: 控制输出顺序



示例：数列计算器 (续1)


- 数据通路

- 输入初始值
- 计算数列
- 输出数列

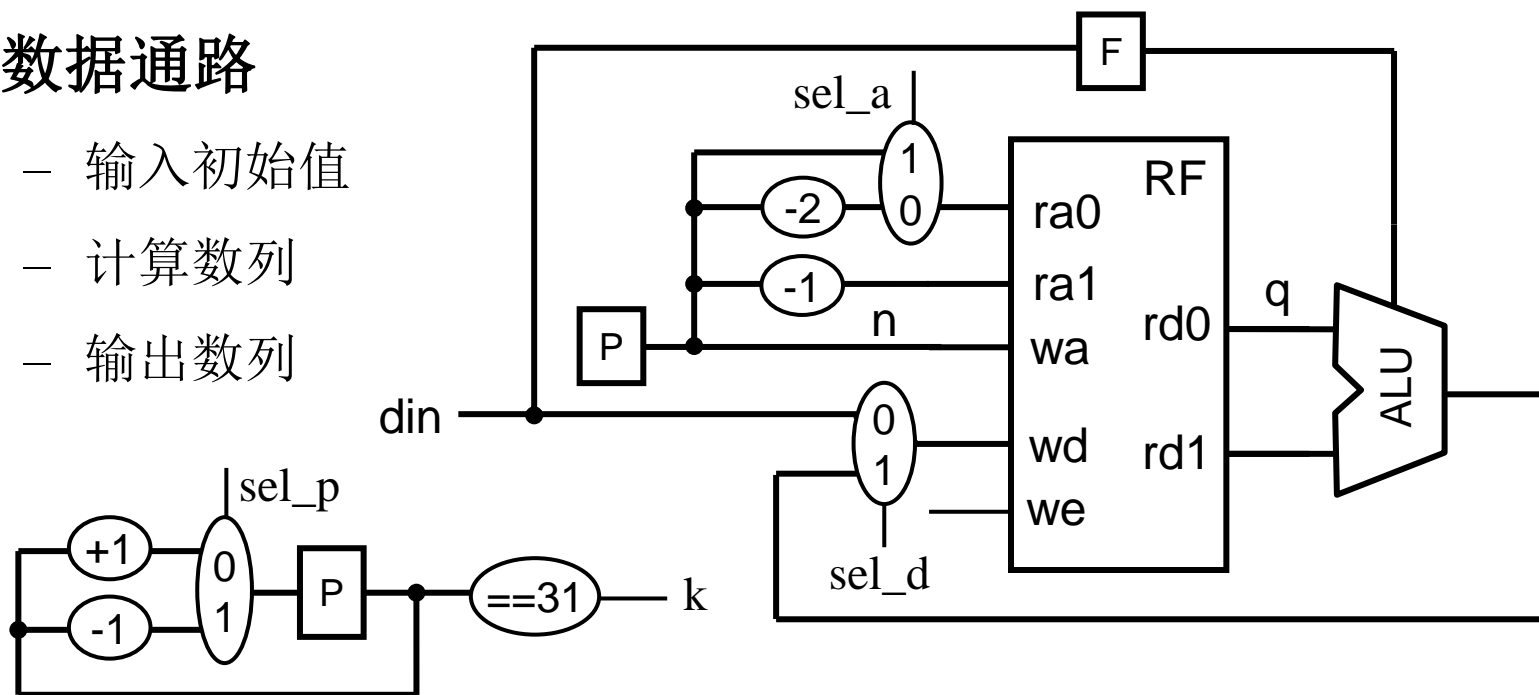


- 控制单元

- en, pri, nxt: 均为单脉冲信号

 

示例：数列计算器 (续2)

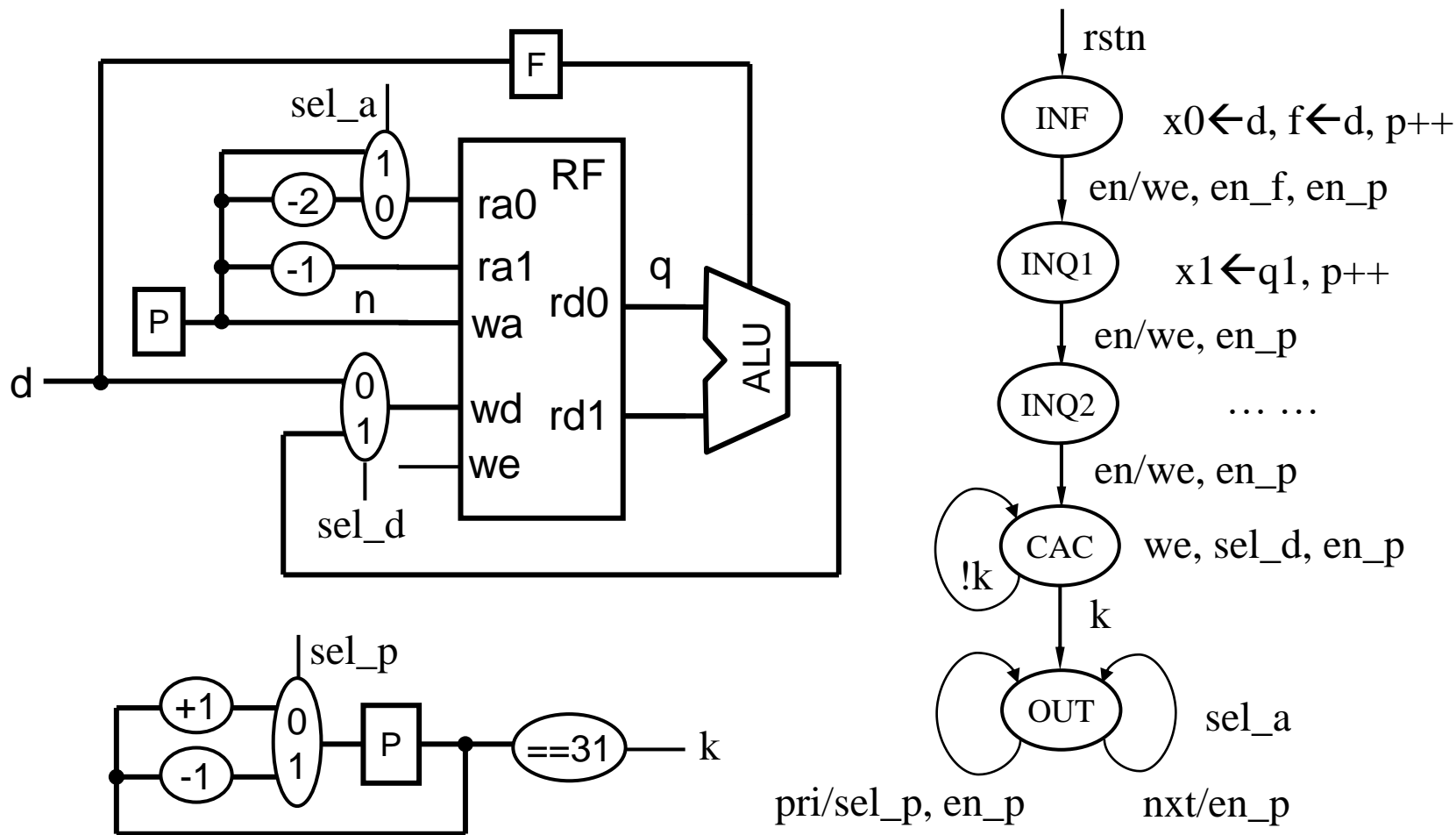

查看电路资源

- 查看Vivado生成电路

- RTL电路: Flow Navigator >> RTL Analysis >> Open Elaborated Design >> Schematic
- 综合/实现电路: Flow Navigator >> Synthesis/Implementation >> Open Synthesized/Implemented Design >> Schematic

- 查看电路资源使用情况

- 综合/实现电路: Flow Navigator >> Synthesis /Implementation >> Open Synthesized/Implemented Design >> Report Utilization

查看电路性能


- 查看综合电路性能

- Flow Navigator >> Synthesis >> Open Synthesized Design >> Report Timing Summary

Name	Slack	Levels	High Fanout	From	To	Total Delay
Path 1	7.713	2	3	A_reg[1]/C	S_reg[3]/D	2.151
Path 2	8.102	1	4	B_reg[0]/C	S_reg[2]/D	1.762
Path 3	8.304	1	4	B_reg[0]/C	S_reg[1]/D	1.560
Path 4	8.597	1	4	A_reg[0]/C	S_reg[0]/D	1.267

示例：加法器

- 8位串行进位加法器： $\{c8, s\} = a + b + c0$;

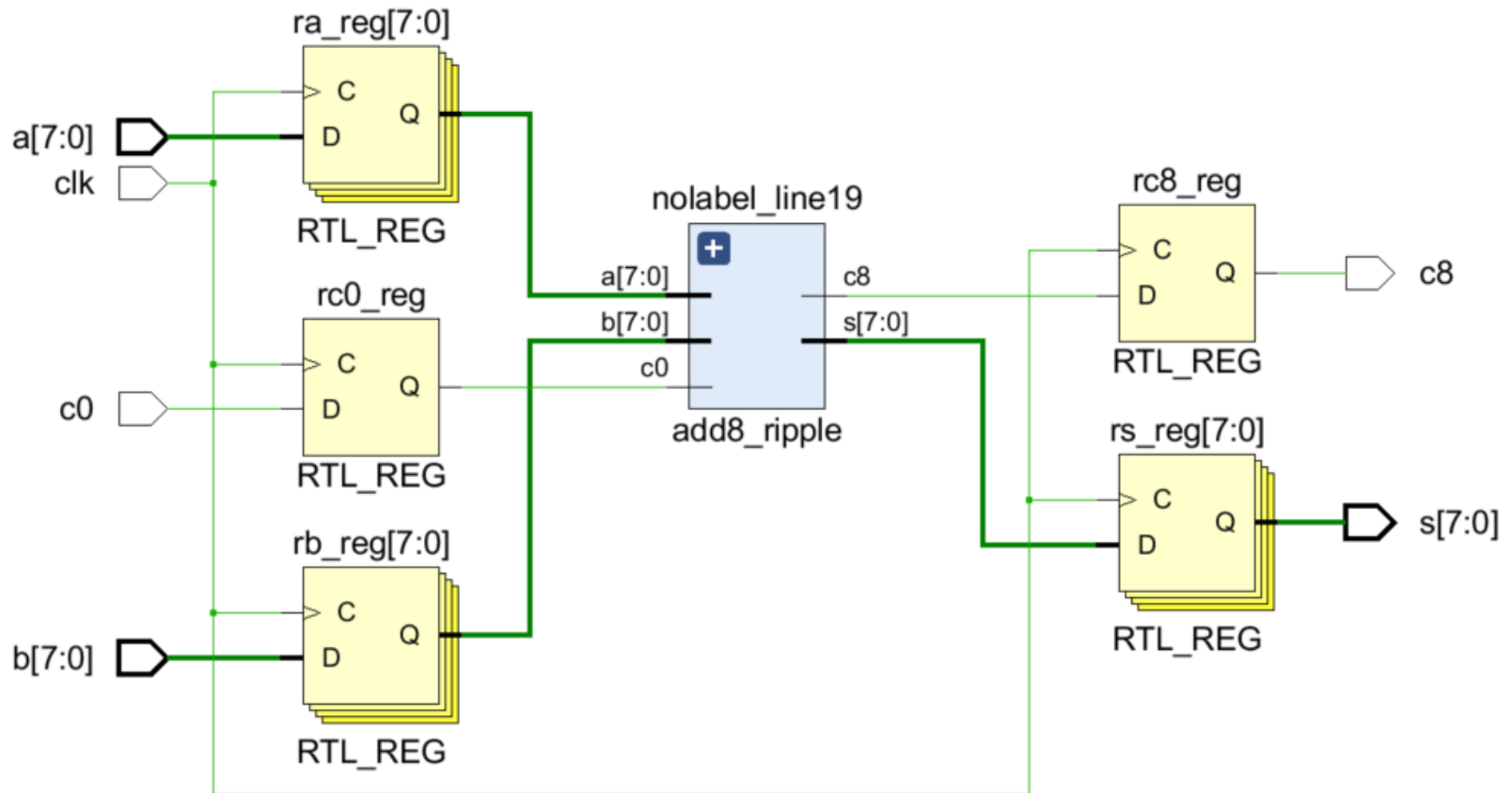

示例：加法器 (续1)

- 设置时钟约束

- 设置尽量高时钟频率，让Vivado工具优化电路和布局

```
set_property -dict { PACKAGE_PIN E3  IOSTANDARD LVCMOS33 }  
[get_ports { clk }];
```

```
create_clock -add -name sys_clk -period 2.00 -waveform { 0 1 } [get_ports  
{ clk }];
```

假设要求电路时钟频率能够达到500MHz

- 查看时序报告

- Report Timing Summary
- 了解电路最长路径和最大延迟
- 若出现红色警示，则表示违反了时钟约束，生成电路的工作速度将可能达不到该频率

示例：加法器 (续2)

Timing

Intra-Clock Paths - sys_clk - Setup

Name	Slack	From	To	Total Delay	Logic Delay	Net Delay	Requirement
Path 1	-0.304	ra_reg[1]/C	rc8_reg/D	2.185	1.704	0.481	2.000
Path 2	-0.228	ra_reg[1]/C	rs_reg[5]/D	2.124	1.643	0.481	2.000
Path 3	-0.222	ra_reg[1]/C	rs_reg[7]/D	2.118	1.637	0.481	2.000
Path 4	-0.147	ra_reg[1]/C	rs_reg[6]/D	2.043	1.562	0.481	2.000
Path 5	-0.123	ra_reg[1]/C	rs_reg[4]/D	2.019	1.538	0.481	2.000
Path 6	-0.001	ra_reg[1]/C	rs_reg[3]/D	1.897	1.416	0.481	2.000
Path 7	0.064	ra_reg[1]/C	rs_reg[2]/D	1.832	1.351	0.481	2.000
Path 8	0.215	ra_reg[0]/C	rs_reg[1]/D	1.681	1.200	0.481	2.000
Path 9	0.390	ra_reg[0]/C	rs_reg[0]/D	1.506	1.025	0.481	2.000

General Information

Timer Settings

Design Timing Summary

Clock Summary (1)

Check Timing (26)

Intra-Clock Paths

sys_clk

Setup -0.304 ns (9)

Hold 0.179 ns (9)

Pulse Width -0.155 ns (9)

Inter-Clock Paths

Other Path Groups

User Ignored Paths

Unconstrained Paths

Timing Summary - timing_1

最长路径：也称关键路径，ra[1] 至 rc8
最大延迟：2.185 ns，其中逻辑延迟1.704 ns，线路延迟0.481 ns
时钟周期：≥ (2 + 0.304) ns

示例：加法器 (续3)

The image shows a timing analysis tool interface. The main window displays a table of Intra-Clock Paths for the clock signal sys_clk. The table lists 9 paths with their respective delays and requirements. A sidebar on the left shows the project hierarchy, with 'sys_clk' selected. A smaller window in the foreground shows the 'Clock Summary' for sys_clk, indicating a period of 2.400 ns and a frequency of 416.667 MHz.

Timing

General Information
Timer Settings
Design Timing Summary
Clock Summary (1)
> Check Timing (26)
v Intra-Clock Paths
v sys_clk
Setup 0.096 ns (9)
Hold 0.179 ns (9)
Pulse Width 0.245 ns (3)
Inter-Clock Paths
Other Path Groups
User Ignored Paths
> Unconstrained Paths

Name	Slack	From	To	Total Delay	Logic Delay	Net Delay	Requirement
Path 1	0.096	ra_reg[1]/C	rc8_reg/D	2.185	1.704	0.481	2.400
Path 2	0.172	ra_reg[1]/C	rs_reg[5]/D	2.124	1.643	0.481	2.400
Path 3	0.178	ra_reg[1]/C	rs_reg[7]/D	2.118	1.637	0.481	2.400
Path 4	0.253	ra_reg[1]/C	rs_reg[6]/D	2.043	1.562	0.481	2.400
Path 5	0.277	ra_reg[1]/C	rs_reg[4]/D	2.019	1.538	0.481	2.400
Path 6	0.399	ra_reg[1]/C	rs_reg[3]/D	1.897	1.416	0.481	2.400
Path 7	0.464	ra_reg[1]/C	rs_reg[2]/D	1.832	1.351	0.481	2.400
Path 8	0.615	ra_reg[0]/C	rs_reg[1]/D	1.681	1.200	0.481	2.400
Path 9	0.790	ra_reg[0]/C	rs_reg[0]/D	1.506	1.025	0.481	2.400


Timing

General Information
Timer Settings
Design Timing Summary
Clock Summary (1)

Name	Waveform	Period (ns)	Frequency (MHz)
sys_clk	{0.000 1.200}	2.400	416.667

示例：加法器 (续4)

- 查看电路资源使用情况：Report Utilization

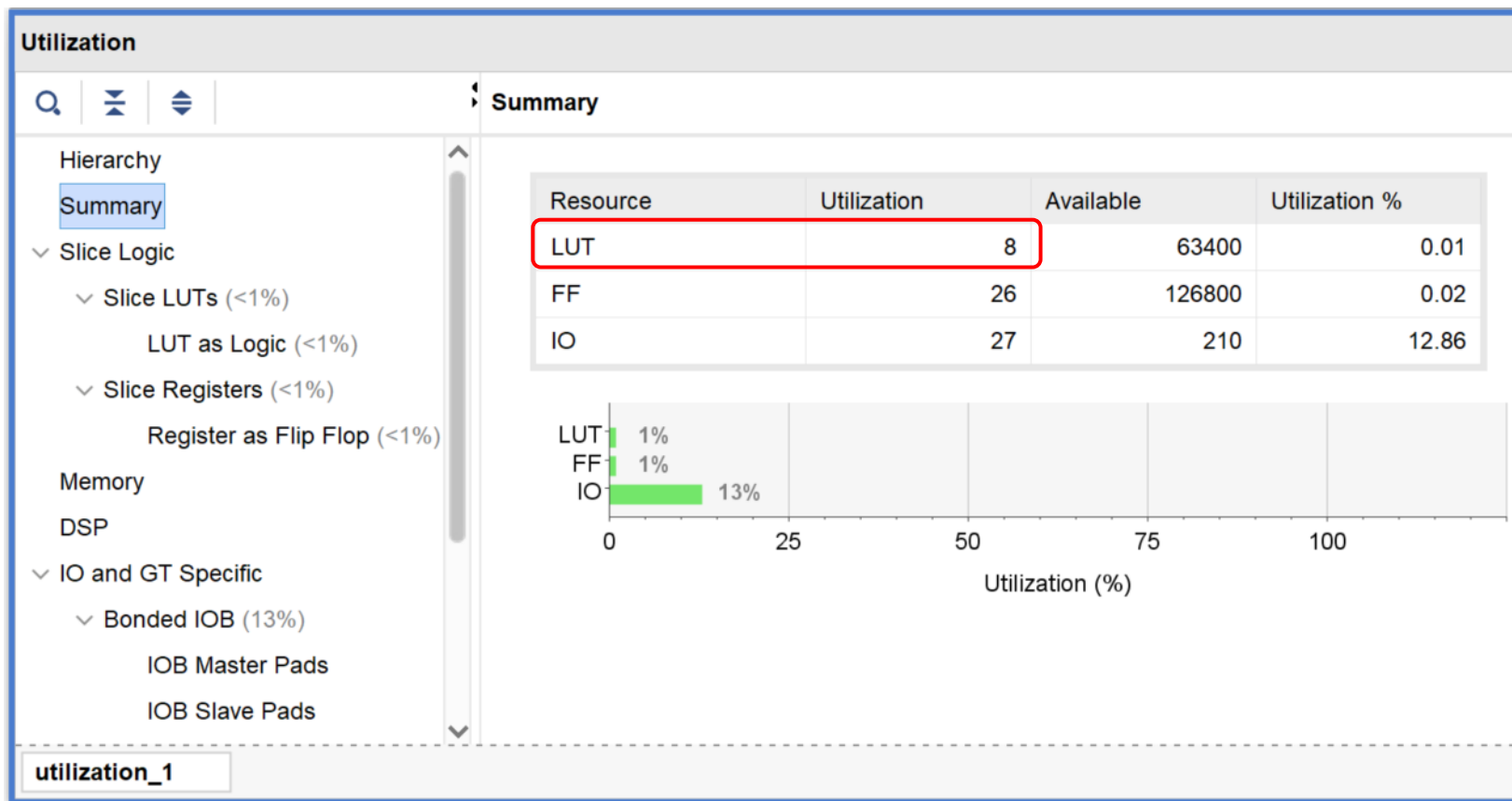

实验要求

- 完成ALU和RF的设计
 - RF的x0内容恒为零，读模式为写优先
 - 查看RTL电路图，综合后功能仿真和查看电路资源
- 比较分布式与块式存储器的特性
 - 单端口RAM存储器，容量1024 x 32位
 - 实现后时序仿真和查看电路资源
- 完成SRT的模块化设计
 - 查看RTL电路图，综合后功能仿真、查看电路资源和性能
 - 下载测试
- 选项
 - 使用块式存储器实现SRT，比较两种实现后的电路资源和性能

The End